

► TASK Demonstrate knowledge of electrical/electronic series, parallel, and series-parallel circuits using principles of electricity (Ohm's Law).

MLR
6A2

AST
6A2

MAST
6A2

CDX Tasksheet Number: C951

Time off: _____

Time on: _____

Total time: _____

NOTE Use Ohm's Law to solve the circuit information in this task.

1. Series Circuit: Circuit Voltage = 12 volts, R1 = 3 ohms, R2 = 9 ohms

a. Draw this circuit in the space below:

- b. Total circuit resistance: _____ ohms
 c. Total circuit current flow: _____ amps
 d. Voltage drop across R1: _____ volts
 e. Voltage drop across R2: _____ volts
 f. Current flow through R1: _____ amps
 g. Current flow through R2: _____ amps

2. Parallel Circuit: Circuit voltage = 12 volts and Branch 1, R1 = 2 ohms and Branch 2, R2 = 4 ohms

a. Draw this circuit in the space below:

- b. Total circuit resistance: _____ ohms
(Hint: $R_t = R_1 \times R_2 / R_1 + R_2$)
 c. Total circuit current flow: _____ amps
 d. Voltage drop across R1: _____ volts
 e. Voltage drop across R2: _____ volts
 f. Current flow through R1: _____ amps
 g. Current flow through R2: _____ amps

3. Series-Parallel Circuit: Circuit voltage = 12 volts, $R_1 = 2$ ohms is in series with the parallel circuit of $R_2 = 3$ ohms and $R_3 = 3$ ohms

a. Draw this circuit in the space below:

b. Total resistance of the parallel circuit: _____ ohms

c. Total circuit resistance: _____ ohms

d. Total circuit current flow: _____ amps

e. Voltage drop across R_1 : _____ volts

f. Voltage drop across R_2 and R_3 : _____ volts

g. Current flow through R_2 : _____ amps

h. Current flow through R_3 : _____ amps

4. Have your supervisor/instructor verify satisfactory completion of this procedure, any observations found, and any necessary action(s) recommended.

Performance Rating

CDX Tasksheet Number: C951

0

1

2

3

4

Supervisor/instructor signature _____ Date _____