

Figure 63.2: an R-C-L network of two loops.

In applying the Laplace transform, we obtain

$$\begin{aligned} \frac{3}{4}(s^2\mathcal{L}[I_1](s) - 2) + \frac{4}{3}(s\mathcal{L}[I_1](s) - s\mathcal{L}[I_2](s)) + \frac{5}{4}\mathcal{L}[I_1](s) &= -\frac{1}{s+1} \\ \frac{4}{3}(s\mathcal{L}[I_2](s) - s\mathcal{L}[I_1](s)) + 4\mathcal{L}[I_2](s) &= 0, \end{aligned}$$

and the corresponding matrix form is

$$\begin{pmatrix} 3s^2/4 + 4s/3 + 5/4 & -4s/3 \\ -4s/3 & 4s/3 + 4 \end{pmatrix} \begin{pmatrix} \mathcal{L}[I_1](s) \\ \mathcal{L}[I_2](s) \end{pmatrix} = \begin{pmatrix} 3/2 - 1/(s+1) \\ 0 \end{pmatrix}.$$

Multiplying both sides with the inverse of the matrix on the left yields

$$\begin{aligned} \mathcal{L}[I_1](s) &= -\frac{2(s+1)/3}{(s+1)^2+4} + \frac{8/3}{(s+1)^2+4} - \frac{2/3}{(s+1)^2} + \frac{2/3}{s+1}, \\ \mathcal{L}[I_2](s) &= \frac{5(s+1)/6}{(s+1)^2+4} + \frac{10/6}{(s+1)^2+4} + \frac{1/3}{(s+1)^2} - \frac{5/6}{s+1}. \end{aligned}$$

Finally, in applying the Laplace inverse transform we find the following solutions:

$$\begin{aligned} I_1(t) &= -\frac{2}{3}e^{-t}\cos(2t) + \frac{4}{3}e^{-t}\sin(2t) - \frac{2}{3}te^{-t} + \frac{2}{3}e^{-t}, \\ I_2(t) &= \frac{5}{6}e^{-t}\cos(2t) + \frac{5}{6}e^{-t}\sin(2t) + \frac{1}{3}te^{-t} - \frac{5}{6}e^{-t}. \end{aligned}$$

63.4. Exercise. Use the exponential-matrix method to verify this result.

63.5. Example. As a somewhat more complicated example, we consider the network of three loops shown in Figure 63.3. The system of differential equations is in this case

$$\begin{aligned} L_1 I_1''(t) + R_1 I_1'(t) + \frac{1}{C_1}(I_1(t) - I_2(t)) &= E_1'(t) \quad (\text{for Loop 1}), \\ L_2(I_2''(t) - I_3''(t)) + R_2 I_2'(t) + \frac{1}{C_1}(I_2(t) - I_1(t)) + \frac{1}{C_2} I_2(t) &= 0 \quad (\text{for Loop 2}), \\ L_2(I_3''(t) - I_2''(t)) + \frac{1}{C_3} I_3(t) &= E_2'(t) \quad (\text{for Loop 3}). \end{aligned}$$

In adding the third equation to the second, it follows that

$$\begin{aligned} L_1 I_1''(t) + R_1 I_1'(t) + \frac{1}{C_1}(I_1(t) - I_2(t)) &= E_1'(t) \\ R_2 I_2'(t) + \frac{1}{C_1}(I_2(t) - I_1(t)) + \frac{1}{C_2} I_2(t) + \frac{1}{C_3} I_3(t) &= E_2'(t) \\ L_2(I_3''(t) - I_2''(t)) + \frac{1}{C_3} I_3(t) &= E_2'(t). \end{aligned}$$

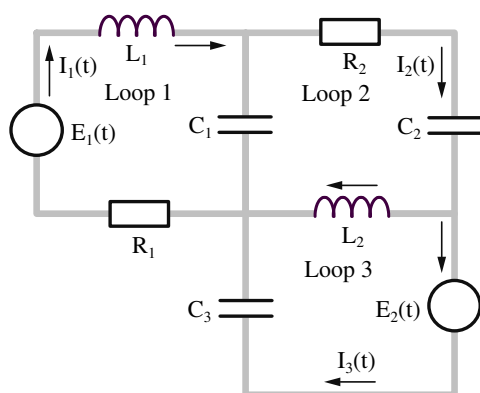


Figure 63.3: an R-C-L network of three loops.

Now introducing the substitutions

$$\begin{aligned} u_1(t) &= I_1(t), \\ u_2(t) &= I_1'(t), \\ u_3(t) &= I_2(t), \\ u_4(t) &= I_2'(t), \\ u_5(t) &= I_3(t), \\ u_6(t) &= I_3'(t), \end{aligned}$$

the equivalent first-order system is easily seen to be

$$\begin{aligned} u_1'(t) &= u_2(t) \\ u_2'(t) &= -\frac{1}{L_1 C_1} u_1(t) - \frac{R_1}{L_1} u_2(t) + \frac{1}{L_1 C_1} u_3(t) + \frac{1}{L_1} E_1'(t) \\ u_3'(t) &= u_4(t) \\ 0 &= \frac{1}{C_1} u_1(t) - \left(\frac{1}{C_1} + \frac{1}{C_2} \right) u_3(t) - R_2 u_4(t) - \frac{1}{C_3} u_5(t) + E_2'(t) \\ u_5'(t) &= u_6(t) \\ u_6'(t) - u_4'(t) &= -\frac{1}{L_2 C_3} u_5(t) + \frac{1}{L_2} E_2'(t). \end{aligned} \tag{63.3}$$

In solving the fourth of these equations for $u_4(t)$, we find that

$$u_4(t) = \frac{1}{R_2 C_1} u_1(t) - \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right) u_3(t) - \frac{1}{R_2 C_3} u_5(t) + \frac{1}{R_2} E_2'(t),$$

and by implication,

$$\begin{aligned} u_4'(t) &= \frac{1}{R_2 C_1} u_1'(t) - \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right) u_3'(t) - \frac{1}{R_2 C_3} u_5'(t) + \frac{1}{R_2} E_2''(t) \\ &= \frac{1}{R_2 C_1} u_2(t) - \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right) u_4(t) - \frac{1}{R_2 C_3} u_6(t) + \frac{1}{R_2} E_2''(t) \\ &= - \left(\frac{1}{R_2^2 C_1^2} + \frac{1}{R_2^2 C_1 C_2} \right) u_1(t) + \frac{1}{R_2 C_1} u_2(t) + \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right)^2 u_3(t) \\ &\quad + \left(\frac{1}{R_2^2 C_1 C_3} + \frac{1}{R_2^2 C_2 C_3} \right) u_5(t) - \frac{1}{R_2 C_3} u_6(t) - \left(\frac{1}{R_2^2 C_1} + \frac{1}{R_2^2 C_2} \right) E_2'(t) + \frac{1}{R_2} E_2''(t). \end{aligned}$$

As we use these results to replace $u_4(t)$ and $u_4'(t)$ in (63.3), the third equation is eliminated and the total number of equations is reduced from six to five:

$$\begin{aligned} u_1'(t) &= u_2(t) \\ u_2'(t) &= -\frac{1}{L_1 C_1} u_1(t) - \frac{R_1}{L_1} u_2(t) + \frac{1}{L_1 C_1} u_3(t) + \frac{1}{L_1} E_1'(t) \\ u_3'(t) &= \frac{1}{R_2 C_1} u_1(t) - \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right) u_3(t) - \frac{1}{R_2 C_3} u_5(t) + \frac{1}{R_2} E_2'(t) \\ u_5'(t) &= u_6(t) \\ u_6'(t) &= -\left(\frac{1}{R_2^2 C_1^2} + \frac{1}{R_2^2 C_1 C_2} \right) u_1(t) + \frac{1}{R_2 C_1} u_2(t) + \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right)^2 u_3(t) \\ &\quad + \left(\frac{1}{R_2^2 C_1 C_3} + \frac{1}{R_2^2 C_2 C_3} - \frac{1}{L_2 C_3} \right) u_5(t) - \frac{1}{R_2 C_3} u_6(t) + \frac{1}{L_2} E_2'(t) \\ &\quad - \left(\frac{1}{R_2^2 C_1} + \frac{1}{R_2^2 C_2} \right) E_2'(t) + \frac{1}{R_2} E_2''(t). \end{aligned}$$

The equivalent matrix form is

$$\begin{pmatrix} u_1'(t) \\ u_2'(t) \\ u_3'(t) \\ u_5'(t) \\ u_6'(t) \end{pmatrix} = \mathbf{A} \begin{pmatrix} u_1(t) \\ u_2(t) \\ u_3(t) \\ u_5(t) \\ u_6(t) \end{pmatrix} + \begin{pmatrix} 0 \\ E_1'(t)/L_1 \\ E_2'(t)/R_2 \\ 0 \\ E_2'(t)/L_2 - (1/C_1 + 1/C_2)E_2'(t)/R_2^2 + E_2''(t)/R_2 \end{pmatrix},$$

where

$$\mathbf{A} = \begin{pmatrix} 0 & 1 & 0 & 0 & 0 \\ -\frac{1}{L_1 C_1} & -\frac{R_1}{L_1} & \frac{1}{L_1 C_1} & 0 & 0 \\ \frac{1}{R_2 C_1} & 0 & -\frac{1}{R_2 C_1} - \frac{1}{R_2 C_2} & -\frac{1}{R_2 C_3} & 0 \\ 0 & 0 & 0 & 0 & 1 \\ -\frac{1}{R_2^2 C_1^2} - \frac{1}{R_2^2 C_1 C_2} & \frac{1}{R_2 C_1} & \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right)^2 & \frac{1}{R_2^2 C_1 C_3} + \frac{1}{R_2^2 C_2 C_3} - \frac{1}{L_2 C_3} & -\frac{1}{R_2 C_3} \end{pmatrix}.$$

63.6. Exercise. Use exponential matrices (and a computer) to solve the first-order system above for $R_1 = 500 \Omega$, $R_2 = 100 \Omega$, $L_1 = 0.1 H$, $L_2 = 0.3 H$, $C_1 = 10^{-6} F$, $C_2 = 2 \cdot 10^{-6} F$, $C_3 = 4 \cdot 10^{-6} F$, $E_1(t) = E_2(t) = \sin(1000t)$, and $I_1(0) = I_2(0) = I_3(0) = I_1'(0) = I_3'(0) = 0$. Note: as in Exercise 63.2, you may again have to work with the formulae in (61.24) or (61.25).

63.7. Example. As our final example in this chapter, we consider the R-C network in Figure 63.4, which does not involve any inductors, but only capacitors and resistors. As in the preceding examples,

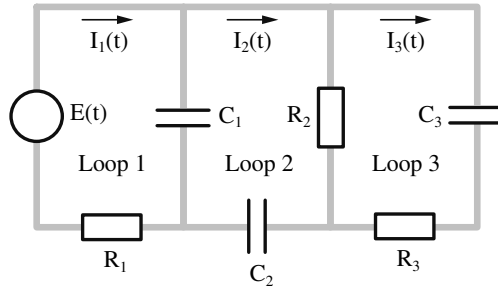


Figure 63.4: an R-C network of three loops.